

**Semester II Examinations, 2003/2004**

Exam Code(s)            2BN1  
                                  2BP1  
Exam(s)                    Second Year Electronic Engineering  
                                  Second Year Electronic and Computer Engineering  
\_\_\_\_\_  
Module Code(s)         EE211  
\_\_\_\_\_  
Module(s)                 Analogue Systems Design I  
\_\_\_\_\_  
Paper No.                 1  
Repeat Paper             \_\_\_\_\_ Special Paper \_\_\_\_\_  
External Examiner(s)    Professor S. McLaughlin  
Internal Examiner(s)    Professor D.J. Wilcox  
                                  Dr. J. Breslin  
                                  Dr. M. Duffy

**Instructions:**            Answer 5 questions.  
                                  All questions carry equal marks.

Duration                 3hrs  
No. of Answer books    1

**Requirements:**         \_\_\_\_\_  
Handout                 \_\_\_\_\_  
MCQ                        \_\_\_\_\_  
Statistical Tables        \_\_\_\_\_  
Graph Paper                Yes  
Log Graph Paper            Yes  
Other Material             \_\_\_\_\_

No. of Pages             6  
Department(s)            Electronic Engineering

1.

(a) For the half-wave rectifier circuit with an ideal diode as shown in Fig. 1:

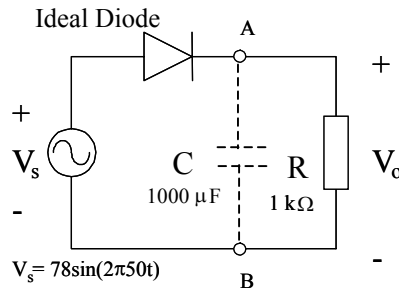


Fig. 1. Half-wave rectifier circuit

- (i) Sketch the output waveform  $V_o$  without the capacitor  $C$  in the circuit. **[2 marks]**
- (ii) Describe the effect on  $V_o$  of placing the capacitor  $C$  in parallel with the load, i.e. between points  $A$  and  $B$  in the circuit. **[3 marks]**
- (iii) Calculate the percentage ripple if  $C$  is included. **[2 marks]**
- (iv) Explain how this circuit could be modified to function as a peak detector. **[2 marks]**

(b) For the Zener diode voltage regulator circuit given in Fig. 2:

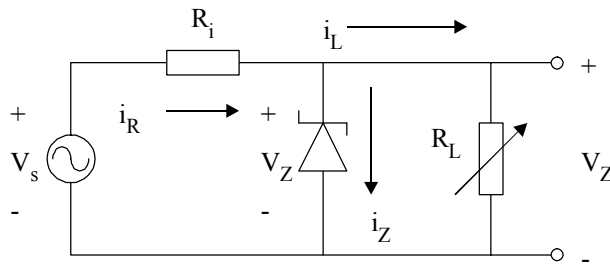


Fig. 2. Zener diode voltage regulator

- (i) Sketch the  $i_D$  vs.  $v_D$  characteristic for a Zener diode showing the various regions of operation. **[2 marks]**
- (ii) In which region does the Zener diode operate for the voltage regulator application shown? **[1 mark]**
- (iii) For varying source voltage and load current, analyse the circuit to determine the proper range of values for  $R_i$  that will allow the diode to maintain a constant output voltage (by keeping the Zener current between its minimum and maximum values). **[6 marks]**
- (iv) Define percentage regulation for the Zener diode voltage regulator. **[2 marks]**

[cont'd]

2.

- (a) Clearly explain the purpose of biasing a transistor. **[3 marks]**
- (b) Using the exact method of calculation, determine the DC values of  $V_B$ ,  $V_C$ ,  $V_E$  and  $I_B$ ,  $I_C$  and  $I_E$  for the BJT in the circuit of Fig. 3. **[7 marks]**

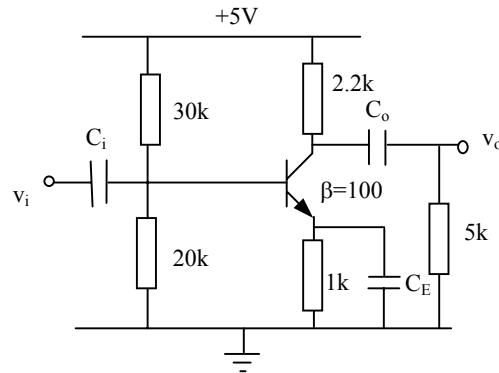


Fig. 3. Common emitter amplifier circuit

- (c) Describe the function of the capacitors  $C_i$  and  $C_o$  in the circuit of Fig. 3. What is the purpose of  $C_E$ ? Calculate the AC voltage gain of the circuit (with the 5k load included). **[8 marks]**
- (d) Plot two periods of the output voltage,  $v_o$ , for a sinusoidal input voltage,  $v_i$ , with 20 mV amplitude. **[2 marks]**

3.

- (a) Describe the semiconductor make-up of an n-channel depletion metal-oxide field effect transistor (D-MOSFET). Clearly explain the depletion mode of operation. **[5 marks]**
- (b) Sketch the typical I-V characteristic curves for an n-channel D-MOSFET, with depletion and enhancement regions clearly marked. **[5 marks]**
- (c) Calculate the DC bias levels for the circuit of Fig. 4 if the MOSFET has values of  $I_{DSS} = 240$  mA and  $V_{GS(off)} = -5$  V. **[10 marks]**

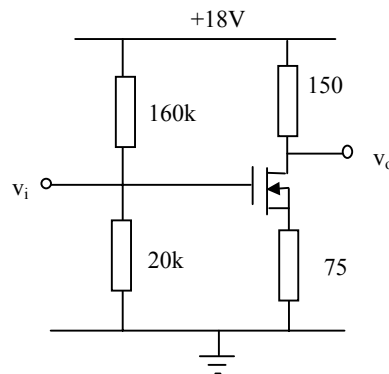


Fig. 4. MOSFET DC biasing circuit

[cont'd]

4.

- (a) Derive an expression for the output voltage,  $v_o$ , in terms of the voltages  $v_1$ ,  $v_2$  and  $v_3$  in the circuit of Fig. 5. State clearly any assumptions made in your derivation. **[4 marks]**

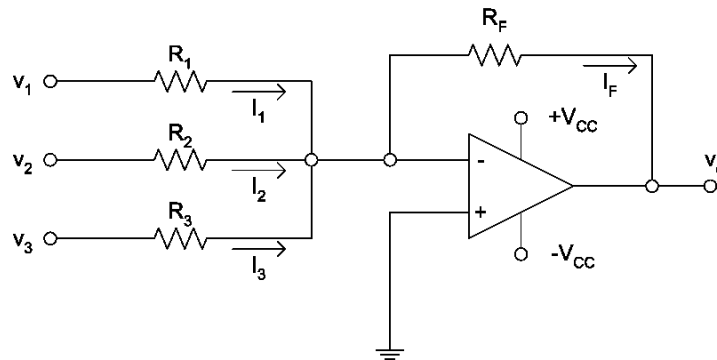


Fig. 5. Op Amp summing circuit

- (b) Give two advantages of active filters over passive filters. Draw the circuit diagram of a first order active high-pass filter and derive the transfer function for the circuit. **[8 marks]**
- (c) Calculate the values of resistor(s) and capacitor(s) required to provide a first order active high-pass filter with cut-off frequency of 2.5 kHz and a pass band gain of 5 ( $A_F = 5$ ). Sketch the frequency response of the resulting filter. **[8 marks]**

5.

- (a) Given that  $I_E = 1$  mA, calculate the following quantities for the Box Model of the amplifier circuit in Fig. 6 : **[8 marks]**

- (i) open circuit gain
- (ii) input resistance
- (iii) output resistance
- (iv) overall system gain

- (b) The transistor in Fig. 6 is a 2N2222 device with parameters :  $C_e = 20.8$  pF,  $C_c = 7.62$  pF and  $\tau_F = 412$  ps. Find the upper and lower 3 dB cutoff frequencies, and sketch the Bode gain plot. **[12 marks]**

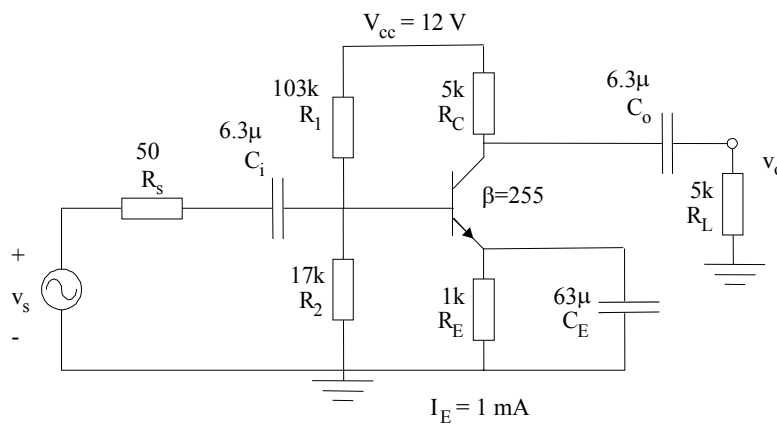


Fig. 6. Common Emitter amplifier circuit

[cont'd]

6.

A moving coil meter with an internal resistance of  $1\text{ k}\Omega$  and a full-scale deflection current rating of  $0.5\text{ mA}$  is to be used in the design of a DC ammeter.

- (a) Describe the circuit required to increase the input current range of the meter. Use this circuit to design an ammeter with input range of  $1\text{ A}$ . **[5 marks]**
- (b) Calculate the total resistance of the ammeter designed in part (a). Determine the percentage error caused by using it to measure  $I_o$  in the circuit of Fig. 7(a). **[4 marks]**

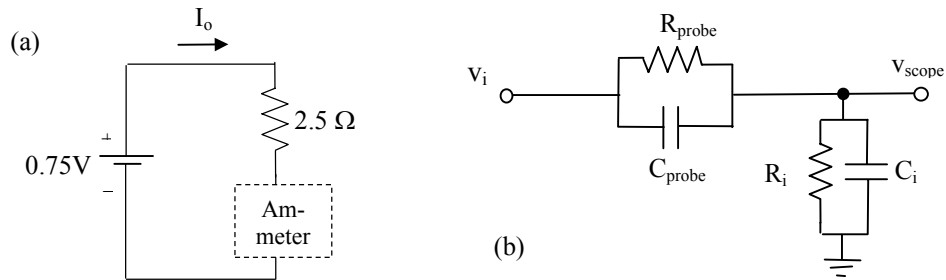


Fig. 7(a) Current test circuit, (b) Circuit model of oscilloscope with probe

The circuit diagram of a  $\times 10$  probe connected to an oscilloscope is shown in Fig. 7(b).

- (c) Explain why  $R_{\text{probe}}C_{\text{probe}}$  must equal  $R_iC_i$  for accurate display of input voltage waveforms. **[6 marks]**
- (d) Design a  $\times 10$  oscilloscope probe with  $R_{\text{total}} = 20\text{ M}\Omega$  and  $C_{\text{total}} = 15\text{ pF}$ . **[5 marks]**

[cont'd]

7.

A resistive strain gauge circuit consists of two active elements and 2 dummy elements as shown in Fig. 8. When subjected to pressure, the strain on both active gauges increases, causing their resistance to increase by  $\Delta R$  as shown.

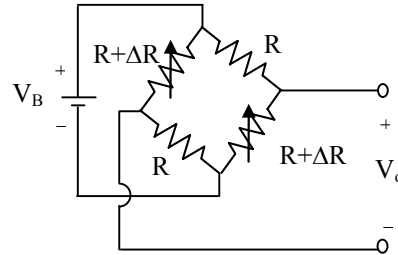


Fig. 8. Strain gauge bridge circuit

- (a) Define what is meant by the following terms as they relate to sensors : **[6 marks]**
- (i) accuracy
  - (ii) range
  - (iii) sensitivity
  - (iv) resolution
- (b) Give two reasons why Wheatstone bridge circuits are used in building sensor circuits. **[4 marks]**
- (c) Answer each of the following for the sensor in Fig. 8 : **[6 marks]**
- (i) Write an expression for the output voltage as a function of  $\Delta R$ ,  $R$  and  $V_B$ .
  - (ii) Calculate the percentage linearity error for  $R = 3.5 \text{ k}\Omega$  and  $\Delta R = 3.5 \Omega$ .
  - (iii) Draw a bridge configuration with zero linearity error. Include an expression for its output voltage
- (d) Draw a block diagram for a sensor circuit that provides a digital output with a current sink. Explain the operation of the current sink. **[4 marks]**